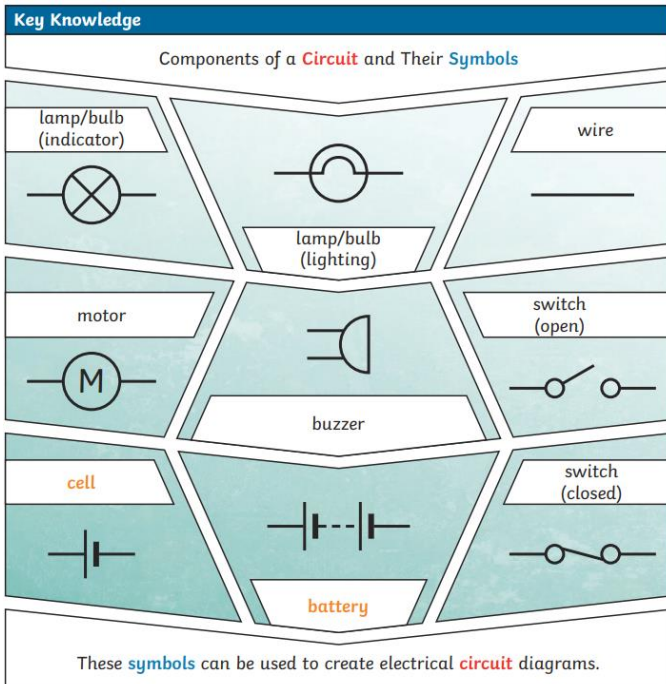


ELECTRICITY – RED SQUIREL CLASS



What will make a bulb brighter or a buzzer louder?

- More **batteries** or a higher **voltage** create more power to flow through the **circuit**.
- Shortening the wires means the electrons have less **resistance** to flow through.

Series Circuit
A **circuit** that has only one route for the **current** to take. If more bulbs or buzzers are added, the power has to be shared and so they will be dimmer or quieter. If just one part of this series **circuit** breaks, the **circuit** is broken and the flow of **current** stops.

What will make a bulb dimmer or a buzzer quieter?

- Fewer **batteries** or a lower **voltage** give less power to the **circuit**.
- More buzzers or bulbs mean the power is shared by more components.
- Lengthening the wires means the electrons have to travel through more **resistance**.

Links to previous learning:

- Scientists and Inventors
- Properties of materials



Important people and places:

- Thomas Edison
- Benjamin Franklin
- Nikola Tesla
- Alexander Graham Bell

circuit	A path that an electrical current can flow around.
symbol	A visual picture that stands for something else.
cell/battery	A device that stores chemical energy until it is needed. A cell is a single unit. A battery is a collection of cells.
current	The flow of electrons, measured in amps.
amps	How electric current is measured.
voltage	The force that makes the electric current move through the wires. The greater the voltage, the more current will flow.
resistance	The difficulty that the electric current has when flowing around a circuit.
electrons	Very small particles that travel around an electrical circuit.